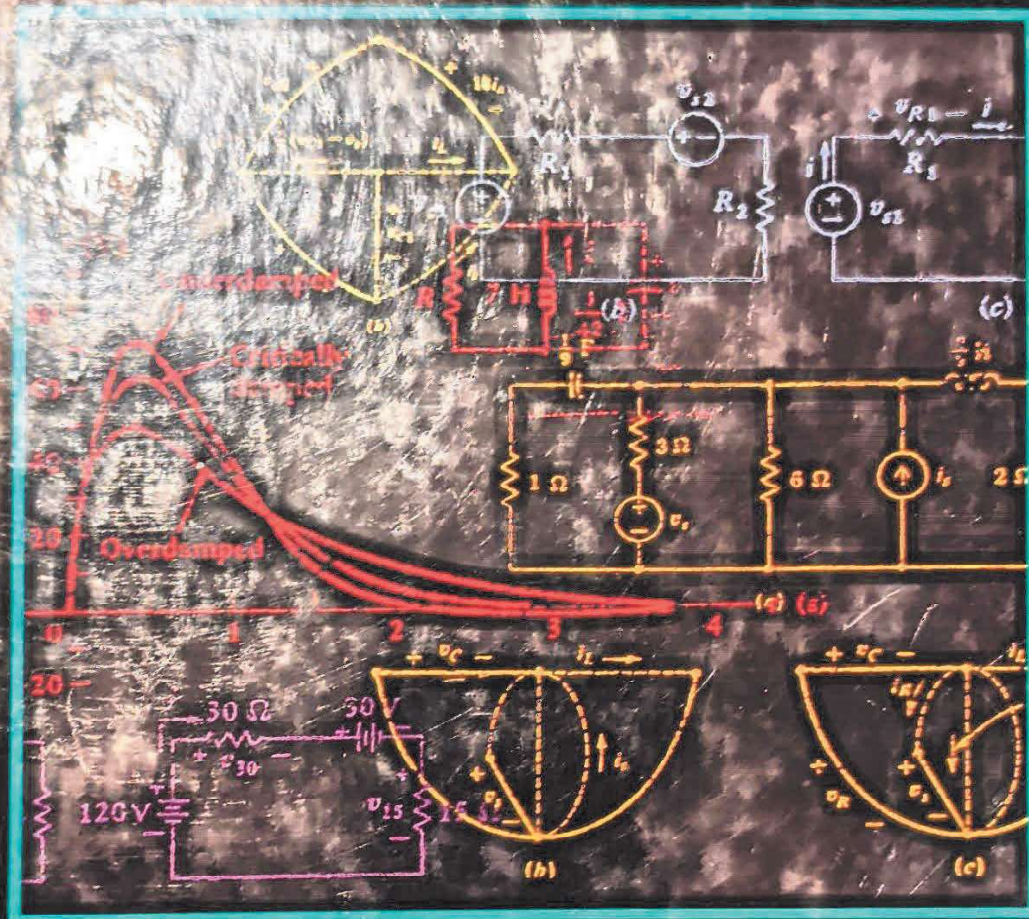


Engineering Circuit Analysis



F I F T H E D I T I O N

WILLIAM H. HAYT, JR. - JACK E. KEMMERLY

ENGINEERING CIRCUIT ANALYSIS

FIFTH EDITION

William H. Hayt, Jr.

Professor of Electrical Engineering, Emeritus
Purdue University

Jack E. Kemmerly

Professor of Engineering, Emeritus
California State University, Fullerton

McGRAW-HILL, INC.

New York St. Louis San Francisco Auckland Bogotá Caracas
Lisbon London Madrid Mexico Milan Montreal New Delhi
Paris San Juan Singapore Sydney Tokyo Toronto

ENGINEERING CIRCUIT ANALYSIS

Copyright © 1993, 1986, 1975, 1971, 1962 by McGraw-Hill, Inc. All rights reserved. Printed in the United States of America. Except as permitted under the United States Copyright Act of 1976, no part of this publication may be reproduced or distributed in any form or by any means, or stored in a data base or retrieval system, without the prior written permission of the publisher.

PSpice is a registered trademark of MicroSim Corporation. All other MicroSim product names are trademarks of MicroSim Corporation. Representations of PSpice/Design Center screens are used by permission of and are proprietary to MicroSim Corporation. Copyright 1992 MicroSim Corporation.

3 4 5 6 7 8 9 0 DOW DOW 9 0 9 8 7 6 5 4

ISBN 0-07-027410-X

*This book was set in Times Roman by Bi-Comp, Inc.
The editors were Anne T. Brown and Jack Maisel;
the designer was Joan Greenfield;
the production supervisor was Kathryn Porzio.
New drawings were done by Fine Line Illustrations, Inc.
R. R. Donnelley & Sons Company was printer and binder.*

Library of Congress Cataloging-in-Publication Data

Hayt, William Hart, (date).

Engineering circuit analysis/William H. Hayt, Jr., Jack E. Kemmerly.—5th ed.

p. cm.—(McGraw-Hill series in electrical and computer engineering. Circuits and systems)

Includes index.

ISBN 0-07-027410-X

1. Electric circuit analysis. 2. Electric network analysis.

I. Kemmerly, Jack E., (date). II. Title. III. Series.

TK454.H4 1993

621.319'2—dc20

92-37799

INTERNATIONAL EDITION

Copyright © 1993. Exclusive rights by McGraw-Hill, Inc. for manufacture and export. This book cannot be re-exported from the country to which it is consigned by McGraw-Hill. The International Edition is not available in North America.

When ordering this title, use ISBN 0-07-112961-8.

Contents

Preface xvii

1 Units, Definitions, Experimental Laws, and Simple Circuits

- 1-1 Introduction 5
- 1-2 Systems of Units 6
- 1-3 Charge, Current, Voltage, and Power 9
- 1-4 Types of Circuits and Circuit Elements 17
- 1-5 Ohm's Law 21
- 1-6 Kirchhoff's Laws 24
- 1-7 Analysis of a Single-Loop Circuit 28
- 1-8 The Single-Node-Pair Circuit 32
- 1-9 Resistance and Source Combination 35
- 1-10 Voltage and Current Division 39
- 1-11 A Practical Example: The Operational Amplifier 42

**Part One:
The Resistive
Circuit**

2 Some Useful Techniques of Circuit Analysis

- 2-1 Introduction 55
- 2-2 Nodal Analysis 55
- 2-3 Mesh Analysis 64
- 2-4 Linearity and Superposition 71
- 2-5 Source Transformations 75
- 2-6 Thévenin's and Norton's Theorems 80
- 2-7 Trees and General Nodal Analysis 88
- 2-8 Links and Loop Analysis 95

**Part Two:
The Transient
Circuit**

3 Inductance and Capacitance

- 3-1 Introduction 115
- 3-2 The Inductor 115
- 3-3 Integral Relationships for the Inductor 119
- 3-4 The Capacitor 124
- 3-5 Inductance and Capacitance Combinations 131
- 3-6 Duality 135
- 3-7 Linearity and its Consequences Again 139

4 Source-free *RL* and *RC* Circuits

- 4-1 Introduction 147
- 4-2 The Simple *RL* Circuit 148
- 4-3 Properties of the Exponential Response 151
- 4-4 A More General *RL* Circuit 154
- 4-5 The Simple *RC* Circuit 157
- 4-6 A More General *RC* Circuit 160

5 The Application of the Unit-Step Forcing Function

- 5-1 Introduction 169
- 5-2 The Unit-Step Forcing Function 169
- 5-3 A First Look at the Driven *RL* Circuit 173
- 5-4 The Natural and the Forced Response 176
- 5-5 *RL* Circuits 178
- 5-6 *RC* Circuits 183

6 The *RLC* Circuit

- 6-1 Introduction 195
- 6-2 The Source-Free Parallel Circuit 196
- 6-3 The Overdamped Parallel *RLC* Circuit 200
- 6-4 Critical Damping 205
- 6-5 The Underdamped Parallel *RLC* Circuit 208
- 6-6 The Source-Free Series *RLC* Circuit 211
- 6-7 The Complete Response of the *RLC* Circuit 215
- 6-8 The Lossless *LC* Circuit 221

7 The Sinusoidal Forcing Function

- 7-1 Introduction 233
- 7-2 Characteristics of Sinusoids 235
- 7-3 Forced Response to Sinusoidal Forcing Functions 237

8 The Phasor Concept

- 8-1 Introduction 245
- 8-2 The Complex Forcing Function 246
- 8-3 The Phasor 250
- 8-4 Phasor Relationships for R , L , and C 254
- 8-5 Impedance 258
- 8-6 Admittance 261

9 The Sinusoidal Steady-State Response

- 9-1 Introduction 269
- 9-2 Nodal, Mesh, and Loop Analysis 269
- 9-3 Superposition, Source Transformations, and Thévenin's Theorem 272
- 9-4 Phasor Diagrams 274
- 9-5 Response as a Function of ω 278

10 Average Power and RMS Values

- 10-1 Introduction 289
- 10-2 Instantaneous Power 290
- 10-3 Average Power 292
- 10-4 Effective Values of Current and Voltage 300
- 10-5 Apparent Power and Power Factor 303
- 10-6 Complex Power 307

11 Polyphase Circuits

- 11-1 Introduction 317
- 11-2 Single-Phase Three-Wire Systems 320
- 11-3 Three-Phase Y-Y Connection 324
- 11-4 The Delta (Δ) Connection 329

Part Three: Sinusoidal Analysis

**Part Four:
Complex
Frequency**

12 Complex Frequency

- 12-1 Introduction 339
- 12-2 Complex Frequency 340
- 12-3 The Damped Sinusoidal Forcing Function 343
- 12-4 $Z(s)$ and $Y(s)$ 346
- 12-5 Frequency Response as a Function of σ 349
- 12-6 The Complex-Frequency Plane 354
- 12-7 Natural Response and the s Plane 363
- 12-8 A Technique for Synthesizing the Voltage Ratio $H(s) = V_{out}/V_{in}$ 369

13 Frequency Response

- 13-1 Introduction 379
- 13-2 Parallel Resonance 380
- 13-3 More about Parallel Resonance 387
- 13-4 Series Resonance 393
- 13-5 Other Resonant Forms 395
- 13-6 Scaling 402
- 13-7 Bode Diagrams 406

**Part Five:
Two-Port
Networks**

14 Magnetically Coupled Circuits

- 14-1 Introduction 427
- 14-2 Mutual Inductance 428
- 14-3 Energy Considerations 435
- 14-4 The Linear Transformer 437
- 14-5 The Ideal Transformer 443

15 General Two-Port Networks

- 15-1 Introduction 459
- 15-2 One-Port Networks 460
- 15-3 Admittance Parameters 463
- 15-4 Some Equivalent Networks 470
- 15-5 Impedance Parameters 478
- 15-6 Hybrid Parameters 483
- 15-7 Transmission Parameters 486

16 State-Variable Analysis

- 16-1 Introduction 503
- 16-2 State Variables and Normal-Form Equations 504
- 16-3 Writing a Set of Normal-Form Equations 507
- 16-4 The Use of Matrix Notation 514
- 16-5 Solution of the First-Order Equation 516
- 16-6 The Solution of the Matrix Equation 520
- 16-7 A Further Look at the State-Transition Matrix 522

Part Six: Signal Analysis

17 Fourier Analysis

- 17-1 Introduction 533
- 17-2 Trigonometric Form of the Fourier Series 535
- 17-3 The Use of Symmetry 541
- 17-4 Complete Response to Periodic Forcing Functions 546
- 17-5 Complex Form of the Fourier Series 549

18 Fourier Transforms

- 18-1 Introduction 561
- 18-2 Definition of the Fourier Transform 561
- 18-3 Some Properties of the Fourier Transform 565
- 18-4 The Unit-Impulse Function 568
- 18-5 Fourier Transform Pairs for Some Simple Time Functions 572
- 18-6 The Fourier Transform of a General Periodic Time Function 577
- 18-7 Convolution and Circuit Response in the Time Domain 578
- 18-8 The System Function and Response in the Frequency Domain 584
- 18-9 The Physical Significance of the System Function 588

19 Laplace Transform Techniques

- 19-1 Introduction 599
- 19-2 Definition of the Laplace Transform 600
- 19-3 Laplace Transforms of Some Simple Time Functions 603
- 19-4 Several Basic Theorems for the Laplace Transform 605
- 19-5 Convolution Again 611
- 19-6 Time-Shift and Periodic Functions 614

- 19-7** Shifting, Differentiation, Integration, and Scaling in the Frequency Domain 619
- 19-8** The Initial-Value and Final-Value Theorems 622
- 19-9** The Transfer Function $H(s)$ 623
- 19-10** The Complete Response 626

Part Seven: Appendixes

Appendix 1/Determinants

Appendix 2/Matrices

Appendix 3/A Proof of Thévenin's Theorem

Appendix 4/Complex Numbers

- A4-1** The Complex Form 653
- A4-2** Euler's Identity 656
- A4-3** The Exponential Form 658
- A4-4** The Polar Form 661

Appendix 5/A SPICE Tutorial

- A5-1** Introduction 665
- A5-2** The dc Analysis: Circuit Elements 665
- A5-3** The dc Analysis: Control and Operating Statements 670
- A5-4** The Transient Analysis: Two More Circuit Elements 672
- A5-5** The Transient Analysis: Time-Varying Sources 672
- A5-6** The Transient Analysis: Operation and Command Statements 673
- A5-7** The ac Analysis: Circuit Elements 676
- A5-8** The ac Analysis: Operation and Command Statements, Single-Frequency Operation 676
- A5-9** The ac Analysis: Analysis Over a Frequency Range 677

Appendix 6/Answers to Odd-Numbered Problems

Index 699

Now that we have added the inductor and capacitor to our list of passive circuit elements, we need to decide whether or not the methods we have developed for resistive circuit analysis are still valid. It will also be convenient to learn how to replace series and parallel combinations of either of these elements with simpler equivalents, just as we did with resistors in Chap. 1.

We look first at Kirchhoff's two laws, both of which are axiomatic. However, when we hypothesized these two laws, we did so with no restrictions as to the types of elements constituting the network. Both, therefore, remain valid.

Now we may extend the procedures we have derived for reducing various combinations of resistors into one equivalent resistor to the analogous cases of inductors and capacitors. We shall first consider an ideal voltage source applied to the series combination of N inductors, as shown in Fig. 3-12a. We desire a

3-5

Inductance and capacitance combinations

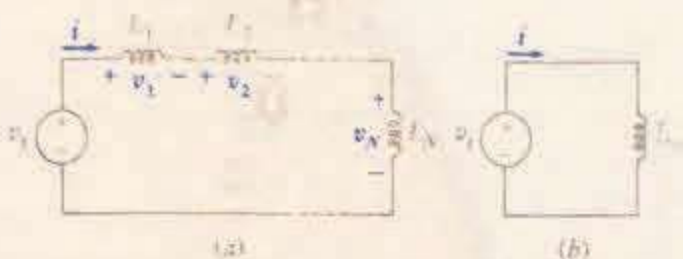


Figure 3-12

(a) A circuit containing N inductors in series. (b) The desired equivalent circuit, in which $L_{eq} = L_1 + L_2 + \dots + L_N$.

single equivalent inductor, with inductance L_{eq} , which may replace the series combination so that the source current $i(t)$ is unchanged. The equivalent circuit is sketched in Fig. 3-12b. For the original circuit,

$$\begin{aligned} v_s &= v_1 + v_2 + \dots + v_N \\ &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\ &= (L_1 + L_2 + \dots + L_N) \frac{di}{dt} \end{aligned}$$

or, written more concisely,

$$v_s = \sum_{n=1}^N v_n = \sum_{n=1}^N L_n \frac{di}{dt} = \frac{di}{dt} \sum_{n=1}^N L_n$$

But for the equivalent circuit we have

$$v_s = L_{eq} \frac{di}{dt}$$

and thus the equivalent inductance is

$$L_{eq} = (L_1 + L_2 + \dots + L_N)$$


or

$$L_{eq} = \sum_{n=1}^N L_n$$

The inductor which is equivalent to several inductors connected in series is one whose inductance is the sum of the inductances in the original circuit. This is exactly the same result we obtained for resistors in series.

Figure 3-13

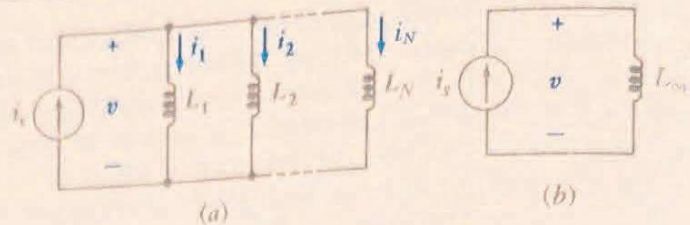(a) The parallel combination of N inductors.
 (b) The equivalent circuit, where $L_{eq} = 1/[(1/L_1) + (1/L_2) + \dots + (1/L_N)]$.



The combination of a number of parallel inductors is accomplished by writing the single nodal equation for the original circuit, shown in Fig. 3-13a,

$$i_s = \sum_{n=1}^N i_n = \sum_{n=1}^N \left[\frac{1}{L_n} \int_{t_0}^t v dt + i_n(t_0) \right]$$

$$= \left(\sum_{n=1}^N \frac{1}{L_n} \right) \int_{t_0}^t v dt + \sum_{n=1}^N i_n(t_0)$$

and comparing it with the result for the equivalent circuit of Fig. 3-13b,

$$i_s = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i_s(t_0)$$

Since Kirchhoff's current law demands that $i_s(t_0)$ be equal to the sum of the branch currents at t_0 , the two integral terms must also be equal; hence,

$$L_{eq} = \frac{1}{1/L_1 + 1/L_2 + \dots + 1/L_N}$$

For the special case of two inductors in parallel,

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

and we note that inductors in parallel combine exactly as do resistors in parallel.

In order to find a capacitor which is equivalent to N capacitors in series, we use the circuit of Fig. 3-14a and its equivalent in Fig. 3-14b to write

$$v_s = \sum_{n=1}^N v_n = \sum_{n=1}^N \left[\frac{1}{C_n} \int_{t_0}^t i dt + v_n(t_0) \right]$$

$$= \left(\sum_{n=1}^N \frac{1}{C_n} \right) \int_{t_0}^t i dt + \sum_{n=1}^N v_n(t_0)$$

and

$$v_s = \frac{1}{C_{eq}} \int_{t_0}^t i dt + v_s(t_0)$$

Figure 3-14

(a) A circuit containing N capacitors in series. (b) The desired equivalent, $C_{eq} = 1/[(1/C_1) + (1/C_2) + \dots + (1/C_N)]$.

